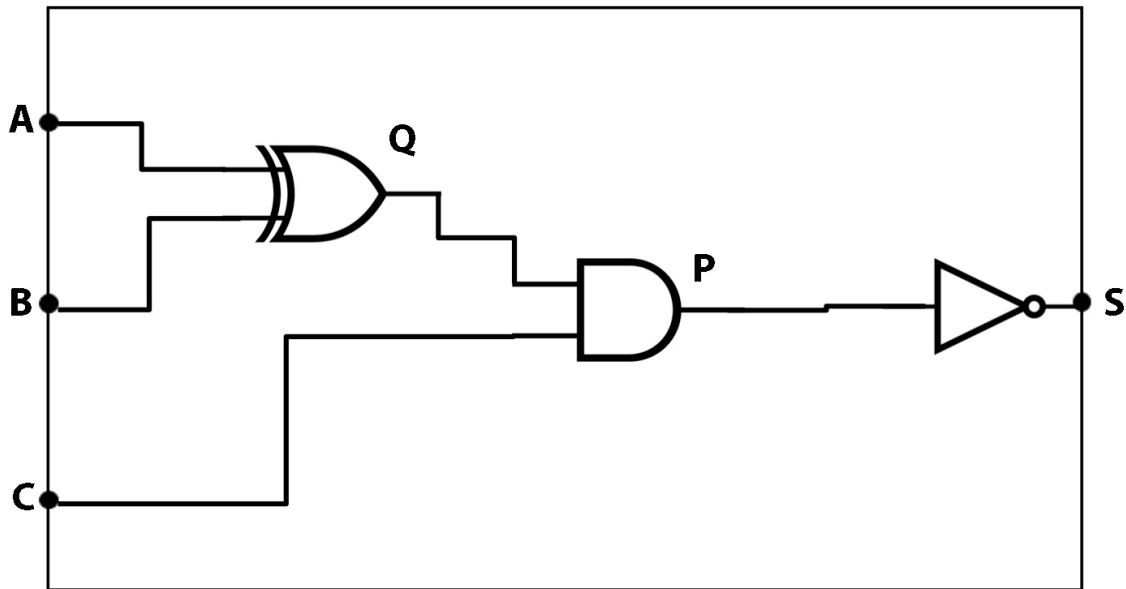


01 A logic circuit is connected as shown. The circuit has three inputs, A, B and C, and one output, S.



01.1 Complete the truth table for the circuit

[3 marks]

| A | B | C | Q | P | S |
|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 |

01.2 Write a word equation for the circuit above

[3 marks]

NOT (C AND (A XOR B))

02 Write the logic statement NOT (A AND B) using logic notation symbols

[2 marks]

(A.B) with an overscore