

# Logic Gates Table

Which gate, or gates:

	Returns True if both inputs are True
	Has only one input
	Returns True if one or both inputs are True
	Has exactly two False outputs
	Has exactly one True output
	Has the most True outputs